



Phantom Blocker

Thank you for purchasing a TritonAudio product!

TritonAudio strives to create innovative audio products which excel in design and quality.

We supply components to the high-end and pro audio community. We wish you lot's of fun with your purchase. Please visit our website (www.tritonaudio.com) to stay informed about new products.

Kind regards,

Team TritonAudio.

Phantom Blocker

Blocks Phantom power not the signal.



Phantom blocker blocks Phantom power while leaving the audio signal intact. Phantom power can be applied to either the male or the female side of Phantom Blocker's xlr connector and will not reach the opposing xlr connector, the audio signal travels without restriction in both directions.

Important

Before connecting the device you wish to shield from Phantom power make sure Phantom blocker is attached (naturally) and have Phantom power switched on. Connecting in this order prevents the transfer of an initial AC voltage burst created by the Phantom power switching on!